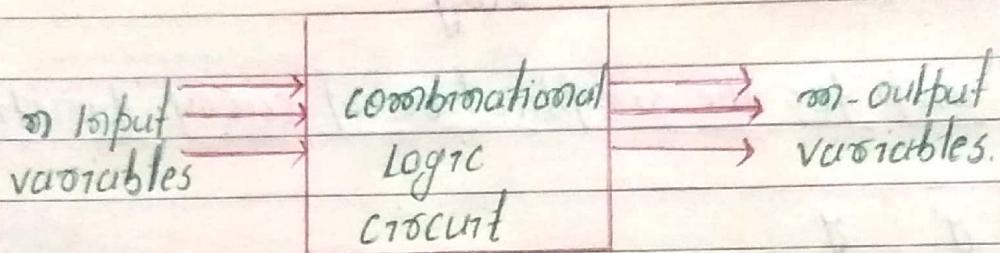


# Combinational logic Circuits:

- A combinational circuit consists of logic gates, they perform a specific information processing operation fully specified logically by a set of Boolean functions.



- m input variables: these  $2^m$  possible combinations of binary inputs. for each possible input combination, there is one and only one possible output combination.
- A combinational circuit can be described by m Boolean functions, one for each output variable.

# Half Adder:

It is a combinational CKT that performs addition of TWO bits.

÷ Truth Table ÷

x	y	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

÷ addition  
1+1 with a carry ①

$\therefore$  K-map for the simplification of sum function

	$y'$	$y$
$x'$	0	1
$x$	1	0

$$\therefore S = x'y + xy' \\ x \oplus y$$

$\therefore$  K-map for the simplification of carry function


	$y'$	$y$
$x'$	0	0
$x$	0	1

$$\therefore C = xy.$$



$\therefore$  Implementation of Half adder

$$S = x'y + xy' \\ x \oplus y$$

$$C = xy$$

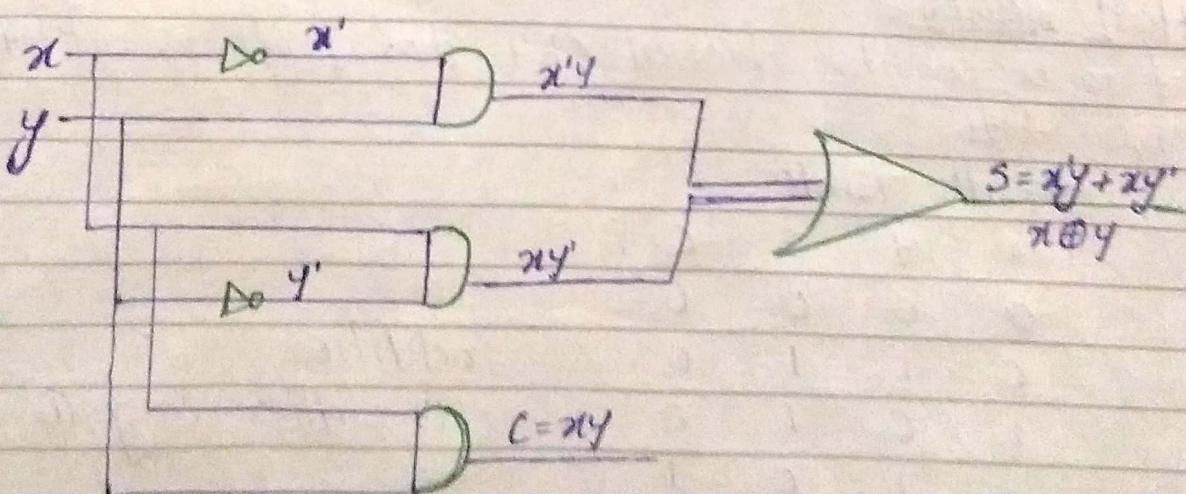

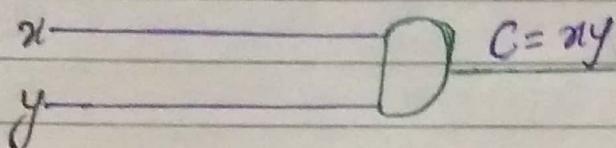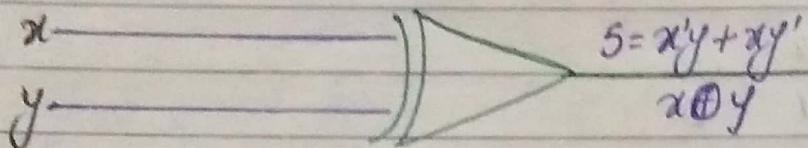÷ Simplification of half adder with EX-OR and AND gate



# FULL adder:

- it is combinational CKT that performs addition of three Bits.

÷ Truth table

$x$	$y$	$z$	$s$	$c$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

÷ K-map for the simplification of sum function ÷

	$y'z'$	$y'z$	$yz$	$yz'$	$\therefore S = x'y'z + x'yz' + xy'z' + xyz$
$x'$	0	1	0	1	$x'[y'z + yz'] + x[y'z' + yz]$
$x$	1	0	1	0	
					$S = x \oplus y \oplus z$

∴ K-map for the simplification of carry function.

	$y_1'$	$y_1$	$y_2'$	$y_2$	
$x'$	0	0	1	0	
$x$	0	1	1	1	

→ Parity.

$$\therefore C = \underline{y_2} + \underline{x_2} + \underline{xy}$$

∴ Implementation of full adder:

$$\begin{aligned} S &= x'y_1' + x'y_1 + xy_1' + xy_1 \\ &= x'[y_1' + y_1] + x[y_1' + y_1] \end{aligned}$$


$$S = \underline{x} \oplus \underline{y} \oplus \underline{2}$$

$$C = \underline{y_2} + \underline{x_2} + \underline{xy}$$

# Design a FULL adder with two Half adders:

- The full-adder must add the two input bits and the input carry.
- The input carry to be added to the input bits, it must be EX-OR with  $A \oplus B$  giving the equation for the sum output of the full adder.


$$S = (A \oplus B) \oplus C$$

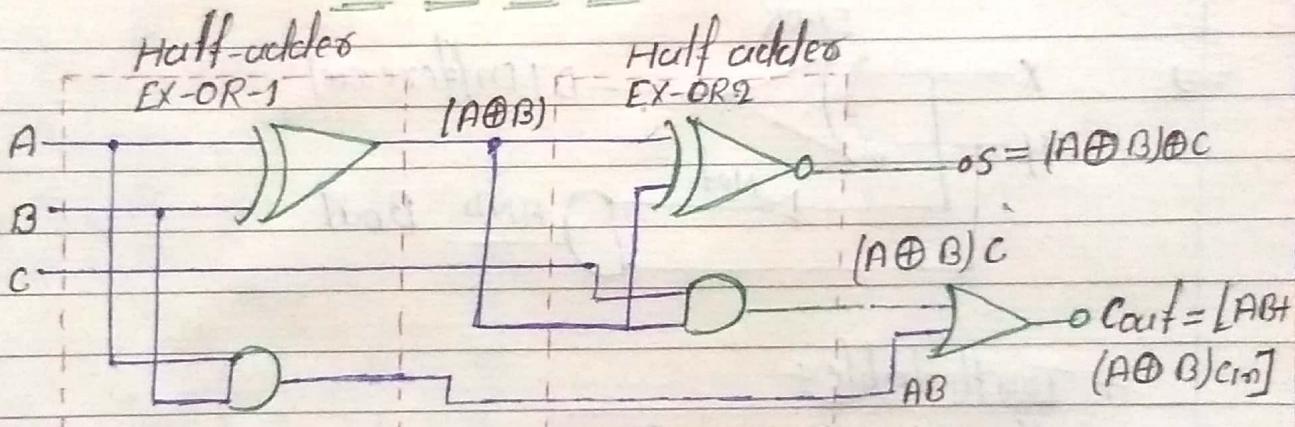

# BINARY Subtractor:



- opposite of the Binary adder. If subtracts two binary no. from each other. The output is Difference [D] and a Borrow [B]

Binary subtractor of two Bits:

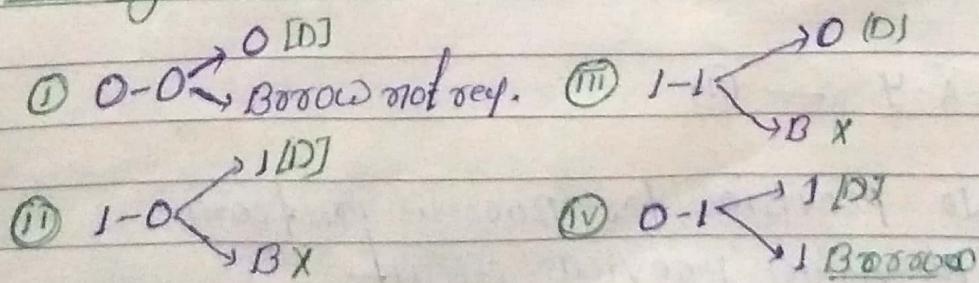

Half Subtractor

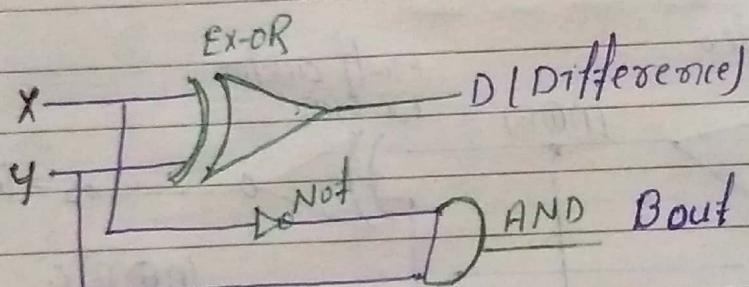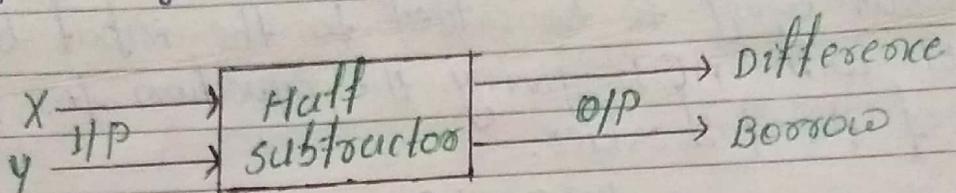- It produces a difference and borrow bits.
- A half subtractor is an arithmetic circuit which is used to perform subtraction of two bits.



÷ Truth table ÷

X	Y	D	B
0	0	0	0
1	0	1	0
0	1	1	1
1	1	0	0

$$D = \bar{X}Y + X\bar{Y}$$


$$X \oplus Y - \textcircled{1}$$

$$B = X \cdot Y - \textcircled{1}$$

Disadv. → No provision for Borrow from previous circuit.

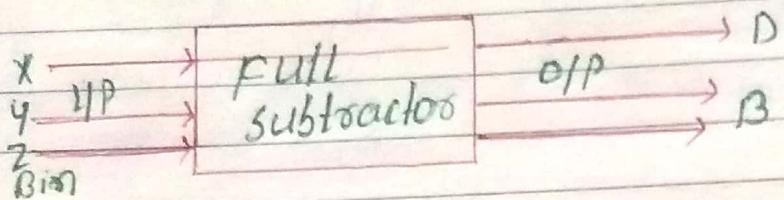
# Full Subtractor:

if has three input, one additional Borrow in (Bin) I/P to receive the Borrow generated by the subtraction process from previous stage input.



÷ Truth Table ÷

Bin	X	Y	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

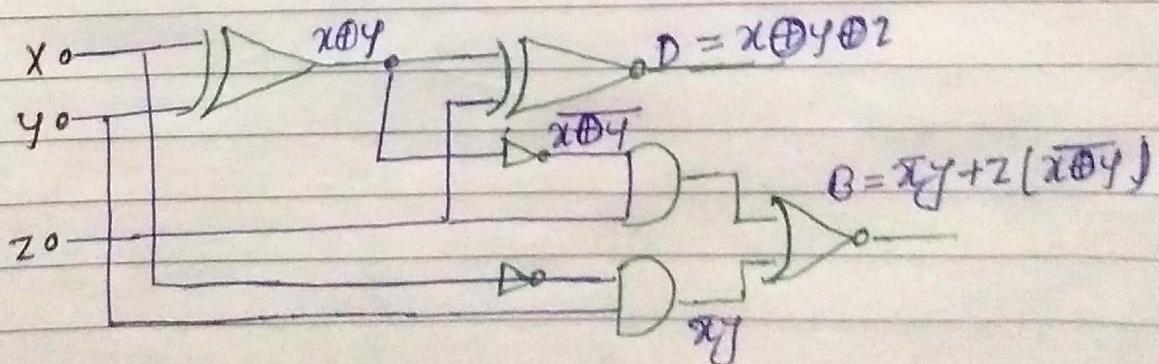


$$D = (X \oplus Y) \oplus B_{\text{in}} \quad \text{--- (1)}$$


$$B_{\text{out}} = (\bar{X} \cdot Y) + (X \oplus Y) B_{\text{in}} \quad \text{--- (2)}$$
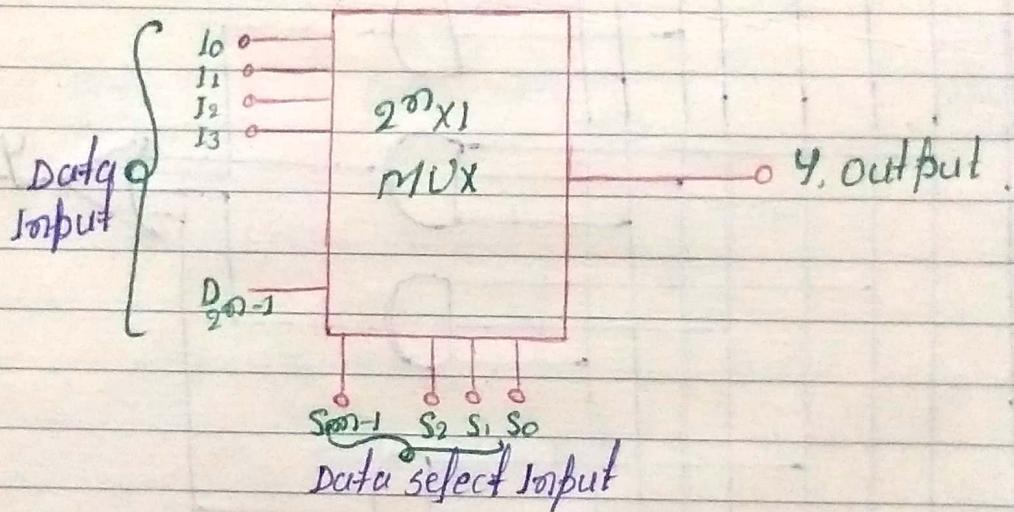
## # Multiplexers : [MUX]

- Multiplexer is a combinational logic circuit used to select only one input among several input based on selection lines.
- This can act as digital switch.
- This is also called as data selector.
- For a MUX there can be  $2^n$  input or selection lines and only one output.



## • Block diagram :

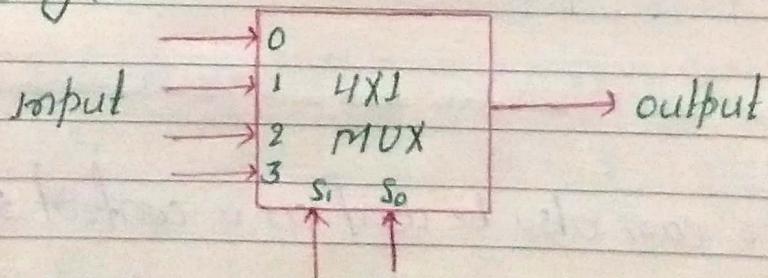


## • Function Table :

	$S_1$	$S_0$	$Y$
	0	0	$I_0$
	0	1	$I_1$
	1	0	$I_2$
	1	1	$I_3$
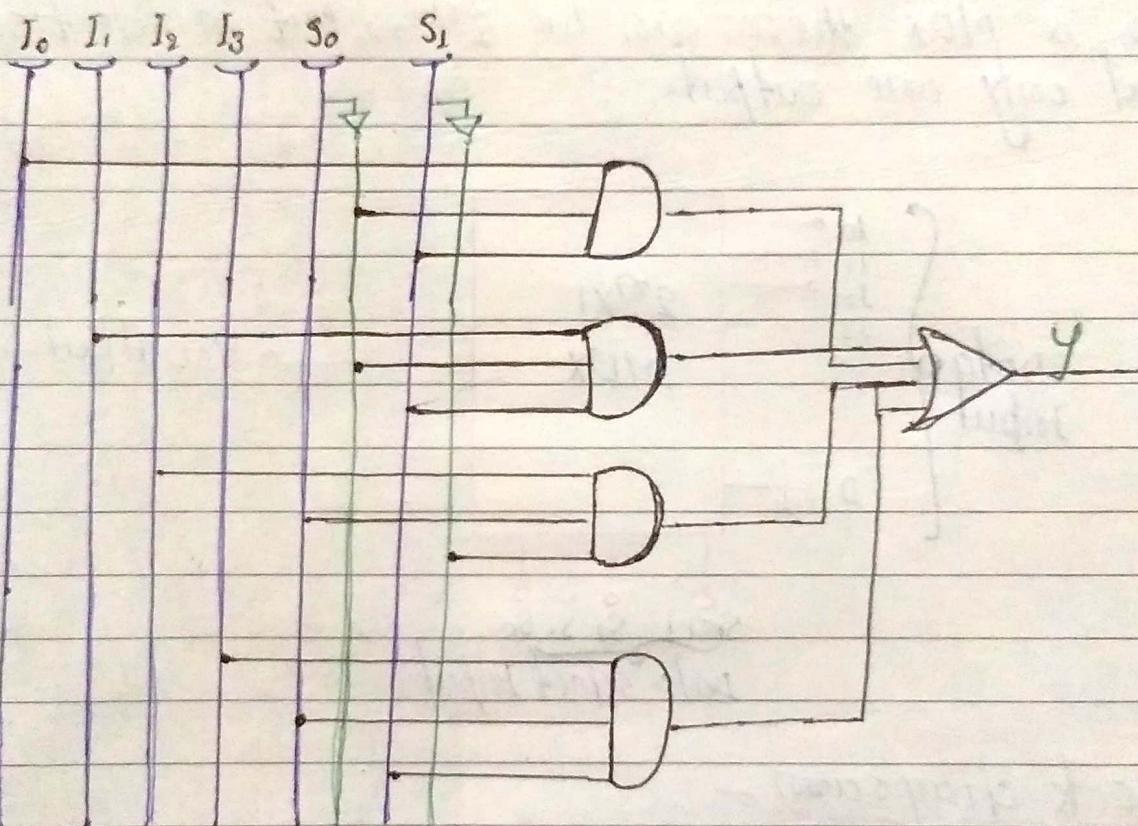
## • Logic Diagram:

$$\begin{aligned}
 y &= D_0 \bar{S}_0 \bar{S}_1 + D_1 \bar{S}_0 S_1 + D_2 S_0 \bar{S}_1 + D_3 S_0 S_1 \\
 &= I_0 \bar{S}_0 S_1 + I_1 S_0 S_1 + I_2 S_0 \bar{S}_1 + I_3 S_0 \bar{S}_1
 \end{aligned}$$




## • Application:

- A multiplexer can also be used as a control sequences.
- A multiplexer can be used for waveform generation.
- The data in parallel form is converted to serial form using multiplexers.

# De-multiplexor:

- It takes a single input line and routes it to one of several digital line.
- 2<sup>n</sup> output has n select lines.
- It is also called data distributor.
- It is opposite of multiplexor.

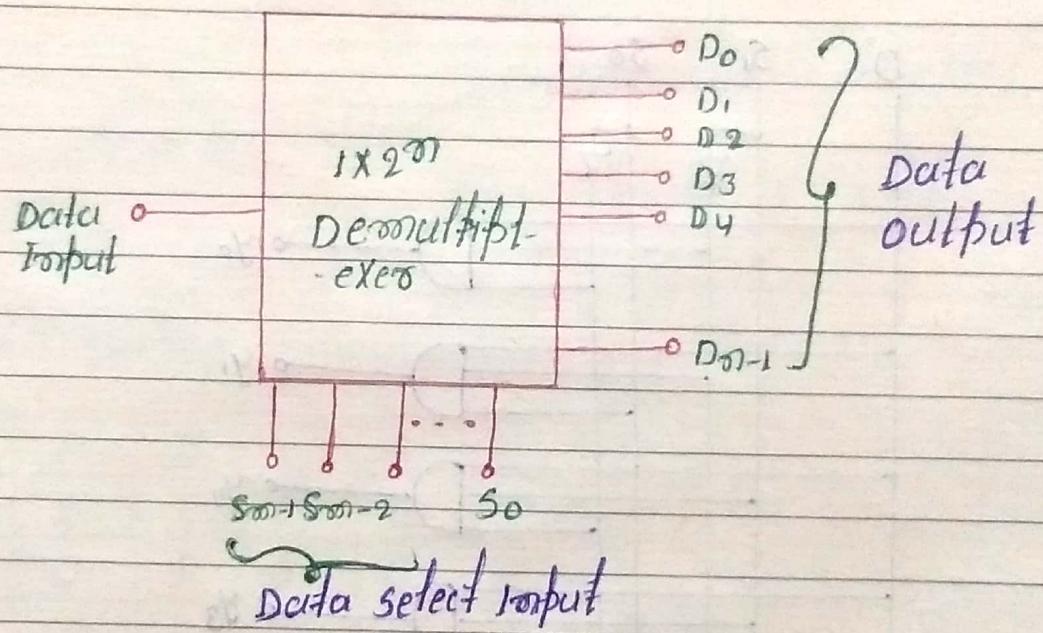• Function Table:

Data In	Data select input		outputs						
D	$S_1$	$S_0$	$y_3$	$y_2$	$y_1$	$y_0$			
1	0	0	0	0	0	1			
1	0	1	0	0	1	0			
1	1	0	0	1	0	0			
1	1	1	1	0	0	0			


- Logic diagram:

$$y_0 = \bar{s}_1 \bar{s}_0 D - \text{I}$$

$$y_1 = \bar{s}_1 s_0 D - \text{II}$$

$$y_2 = s_1 \bar{s}_0 D - \text{III}$$

$$y_3 = s_1 s_0 D - \text{IV}$$

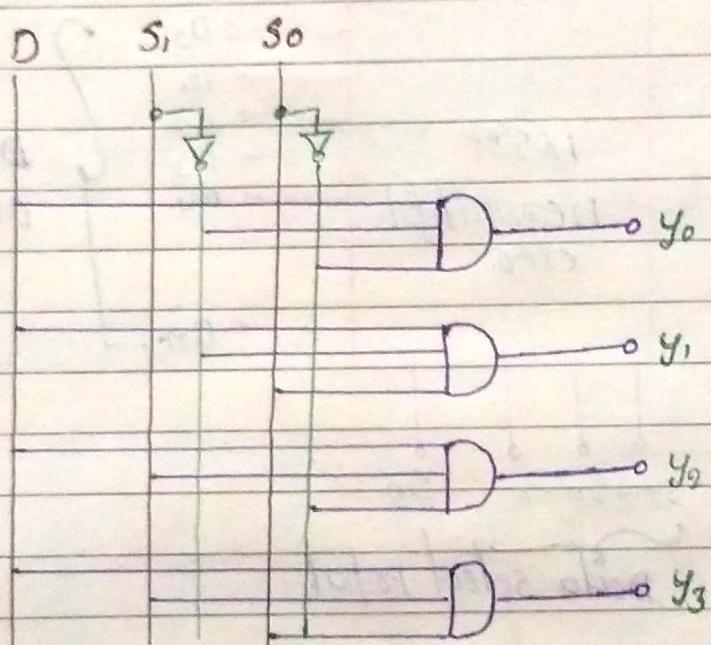


- Application:

Demultiplexers are used as clock demultiplexers in synchronous data transmission systems in the receivers and security monitoring systems etc.

- This device is very useful if multiple output combinational circuit is to be designed.
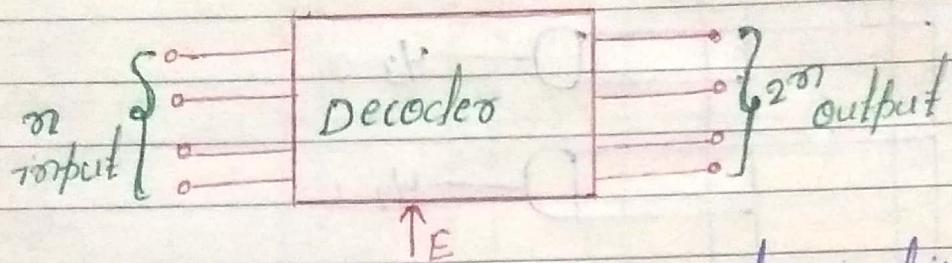
# Decoder:

Decoder is a multi-input multi-output logic circuit which decodes n input into  $2^n$  possible output.



where  $E = \text{Enable}$

- $\rightarrow E=0$  [Decoder is disable]
- $\rightarrow E=1$  [Decoder is enable]

✳ 2 to 4 Decoder

E	A	B	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	X	X	0	0	0	0
1	0	0	0	0	0	1
	0	1	0	0	1	0
	1	0	0	1	0	0
	1	1	1	0	0	0


$$Y_0 = \bar{A}\bar{B} \quad ? \quad Y$$

$$Y_1 = \bar{A}B$$

$$Y_2 = A\bar{B}$$

$$Y_3 = AB$$

④ logic diagram :

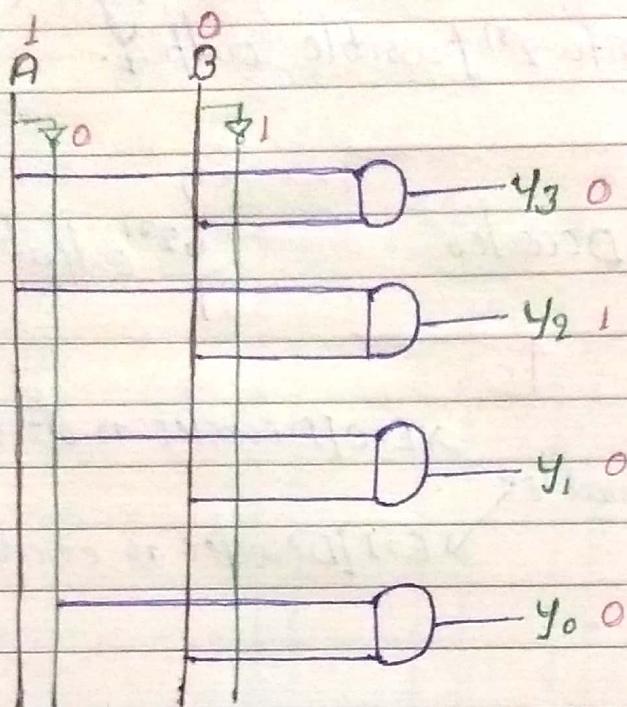

④ Application :

- They are used in analog to digital converters.
- Decoder output can be used to drive a display system.

④ 3 to 8 line decoder

A	B	C	y7	y6	y5	y4	y3	y2	y1	y0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

(\*) logic diagram:

$$y_7 = ABC$$

$$y_6 = A\bar{B}C$$

$$y_5 = A\bar{B}\bar{C}$$


$$y_4 = A\bar{B}C$$

$$y_3 = \bar{A}BC$$

$$y_2 = \bar{A}B\bar{C}$$

$$y_1 = \bar{A}\bar{B}C$$

$$y_0 = \bar{A}\bar{B}\bar{C}$$

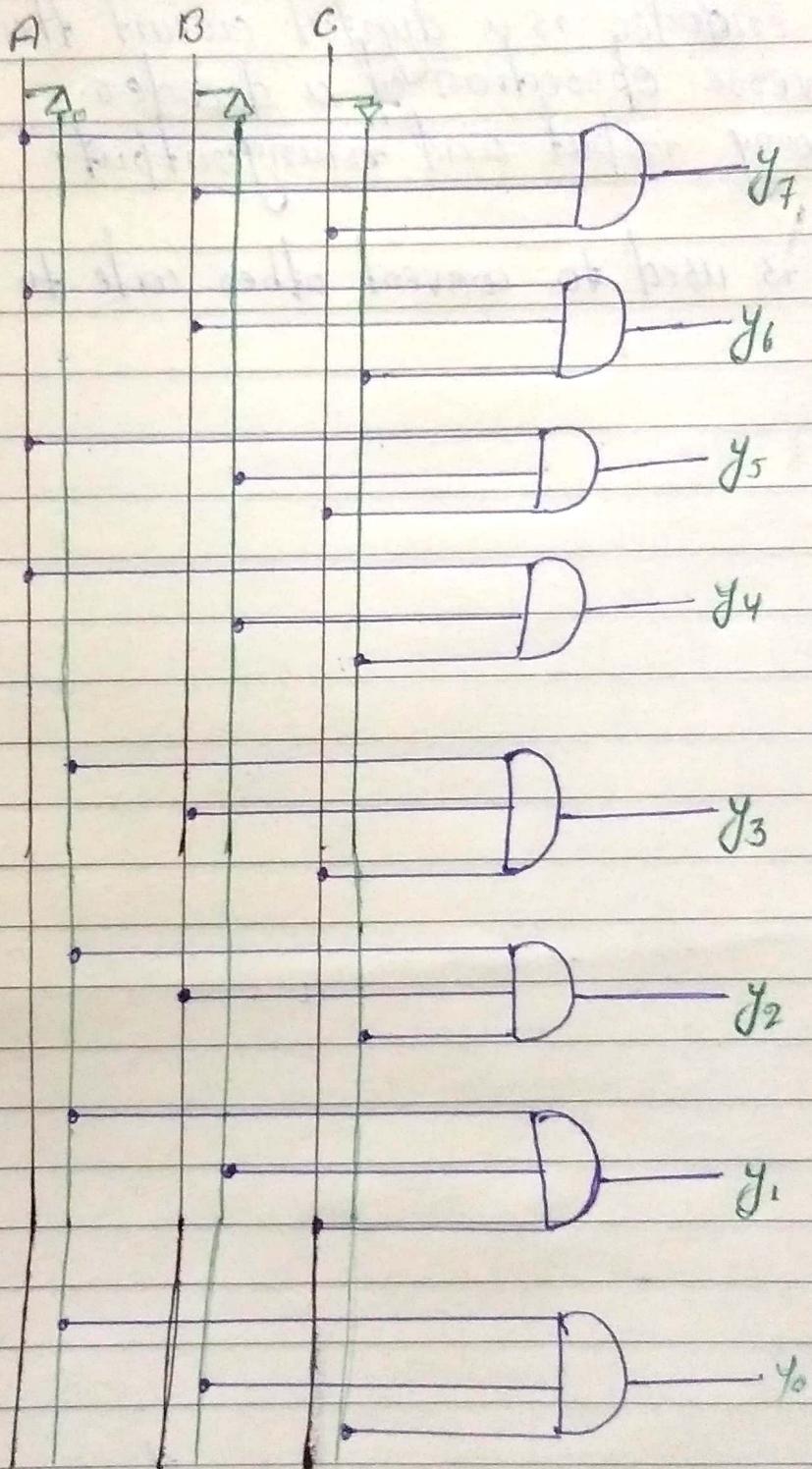

#

Encoder:

- An encoder is a digital circuit that performs the inverse operation of a decoder.
- many input and many output.
- it is used to convert other code to binary.